

EEE 303: Digital Electronics

Total Marks: 20

Time: 15 minutes

Student Number:

Date:

1. A circuit with two outputs has to implement the following functions

$$f(x_1, x_2, x_3, x_4) = \sum m(4, 6, 7, 9, 11, 12, 14, 15) + D(1, 3)$$

$$g(x_1, x_2, x_3, x_4) = \sum m(1, 4, 9, 12) + D(3, 6, 14)$$

Design the minimum cost circuit and compare its cost with combined costs of two circuits that implement f and g separately. Assume that the input variables are available both in uncomplemented and complemented forms.

20

EEE 303: Digital Electronics

Total Marks: 20

Time: 20 minutes

Student Number:

Date:

SET – A

1. A combinational circuit is defined by the following three functions:

i. $F_1 = x'y' + xyz'$

ii. $F_2 = x' + y$

iii. $F_3 = xy + x'y'$

Design the circuit with **only a decoder with an enabler pin and some external gates**.

2. Construct the truth table for a 4 to 2 input priority encoder with input priorities **w₁**, **w₂**, **w₀**, **w₃** where **w₁ has the highest priority and w₃ has the lowest**. The output binaries are denoted as **y₀** and **y₁**. Now, design the circuit for the encoder **using only 4 to 1 multiplexers**.

Class Test 2

EEE 303: Digital Electronics

Total Marks: 20

Time: 20 minutes

Student Number:

Date:

SET – B

1. Construct the truth table for a 4 to 2 input priority encoder with input priorities **w₁, w₃, w₀, w₂** where **w₁ has the highest priority and w₃ has the lowest**. The output binaries are denoted as **y₀** and **y₁**. Now, design the circuit for the encoder **using only 4 to 1 multiplexers**.
2. A combinational circuit is defined by the following three functions:
 - i. **$F_1 = x' + y$**
 - ii. **$F_2 = x'y' + xy$**
 - iii. **$F_3 = xyz' + x'y'$**

Design the circuit with **only a decoder with an enabler pin** and **some external gates**.

EEE 303: Digital Electronics


Total Marks: 20

Time: 20 minutes

Student Number: _____ Date: _____

SET – A

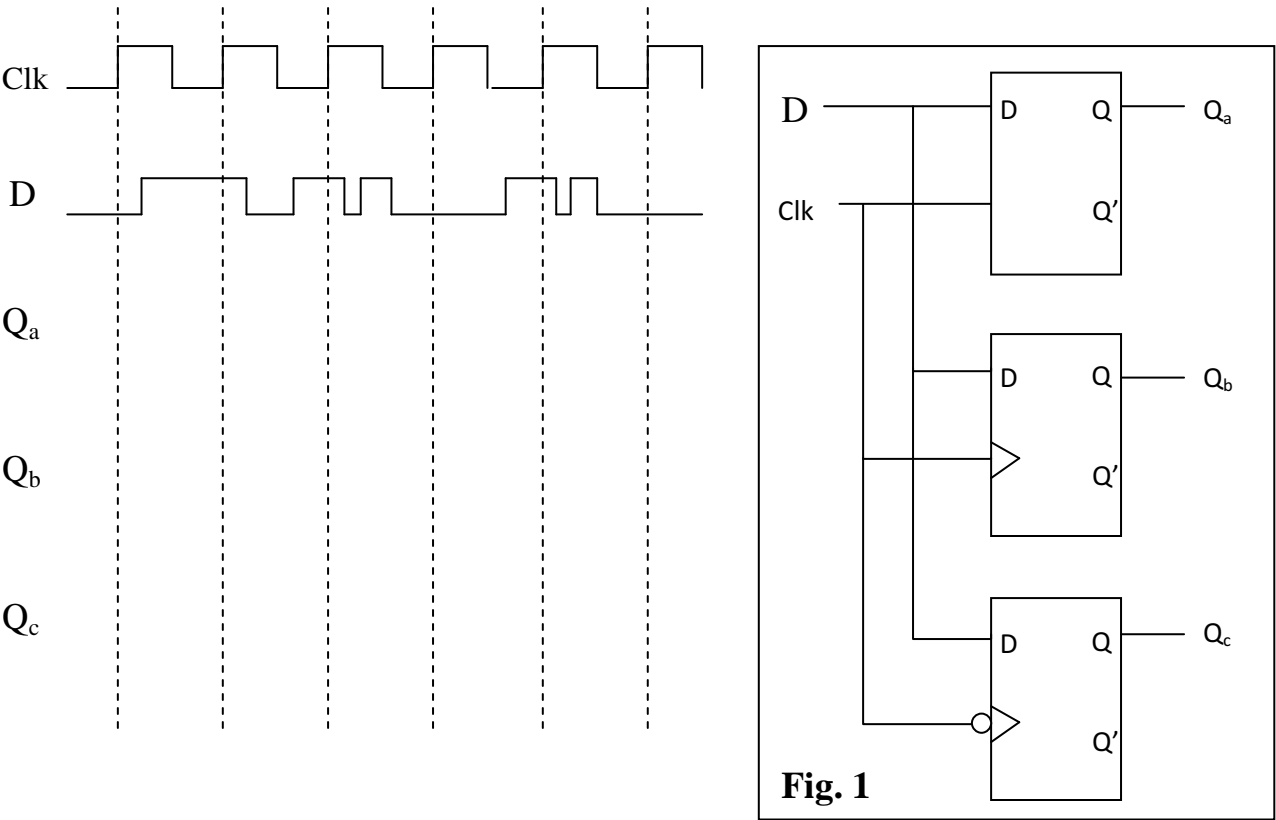1. Consider the following timing diagram. Assume that the D and Clock inputs are applied to the circuit in Fig. 1, draw waveform for the Q_a , Q_b and Q_c signals.



2. Draw the circuit diagram of a three bit shift register using JK flip flops only.

EEE 303: Digital Electronics

Total Marks: 20


Time: 20 minutes

Student Number:

Date:

SET – B

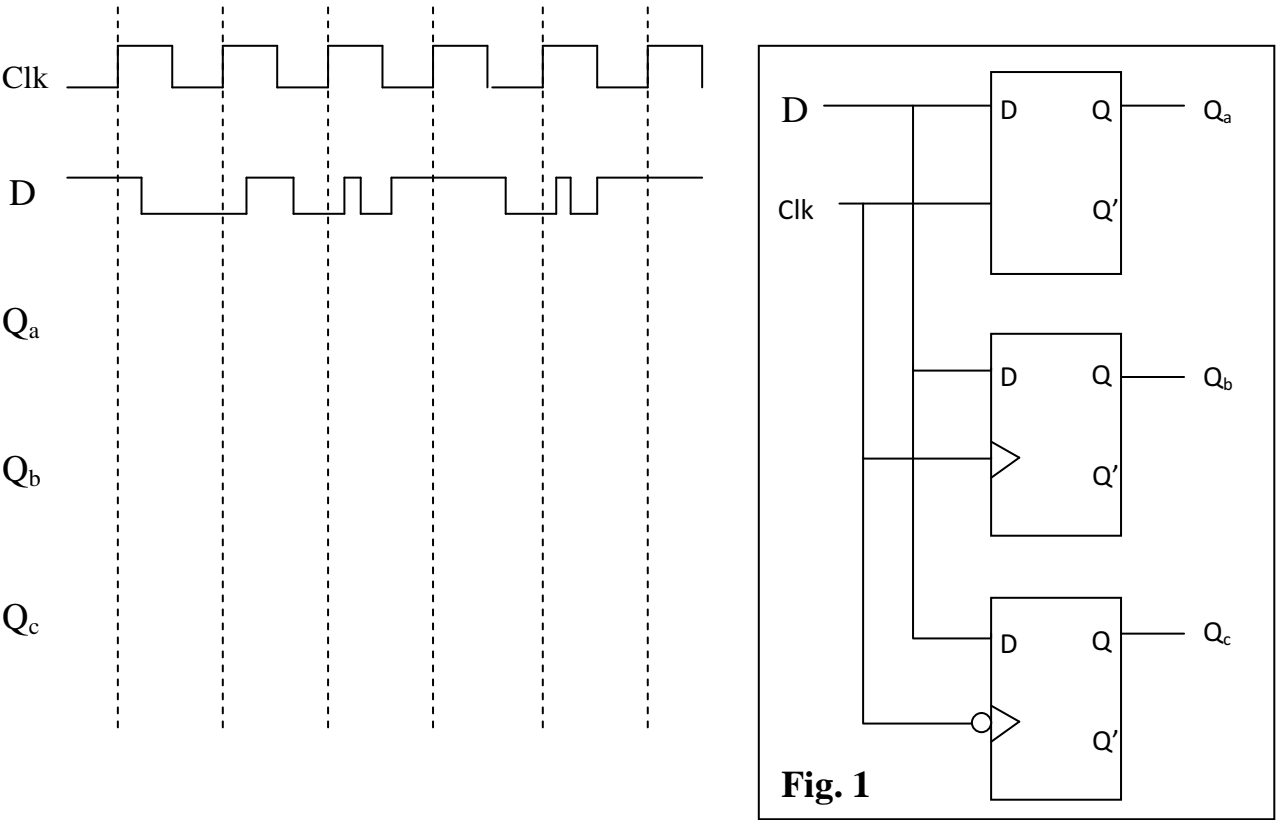1. Consider the following timing diagram. Assume that the D and Clock inputs are applied to the circuit in Fig. 1, draw waveform for the Q_a , Q_b and Q_c signals.



2. Draw the circuit diagram of a three bit shift register using JK flip flops only.

Class Test 4

EEE 303: Digital Electronics

Total Marks: 20

Time: 20 minutes

Student Number:

Date:

1. Using an ordinary 4-bit binary up counter and basic logic gates construct a 4-bit binary counter that counts in the sequence:
1, 3, 6, 9, C, D, 1, 3, 6, 9, C, D...